

ELECTRICAL/ELECTRONIC SYSTEMS


UNIT 2: ELECTRICAL CIRCUITS

LESSON 1: COMPONENTS OF AN ELECTRICAL CIRCUIT


I. Factors that influence resistance

A. The five factors that determine the resistance of conductors are length, diameter, temperature, physical condition, and conductor material. A light bulb filament, motor windings or coil windings, and the bimetal elements in sensors are conductors. Also, the five factors apply to circuit wiring and working devices or loads.

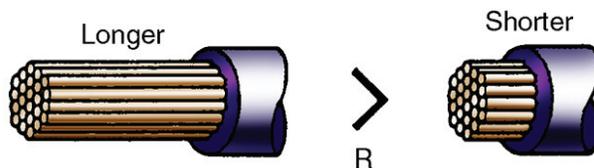1. When two wires consist of the same material and diameter, the longer wire has greater resistance than the shorter wire. Wire resistance is listed in ohms per foot. Replacement wires must be the proper length.



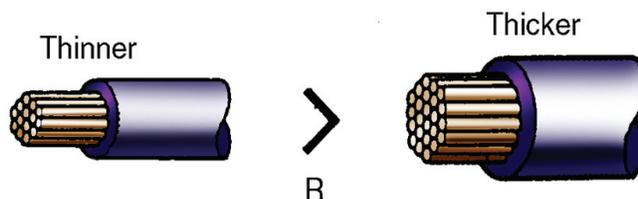
2. If two wires are the same material and length, the thinner wire has greater resistance than the thicker wire. Wire resistance tables list ohms per foot for wires of various thicknesses. Replacement wires and splices must be the proper size for the circuit current.




NOTE: Consider size and gauge when replacing wires. Those with 1, 2, and 3 are thicker with less resistance and more current capacity while those with 18, 20, and 22 are thinner with more resistance and less current capacity.



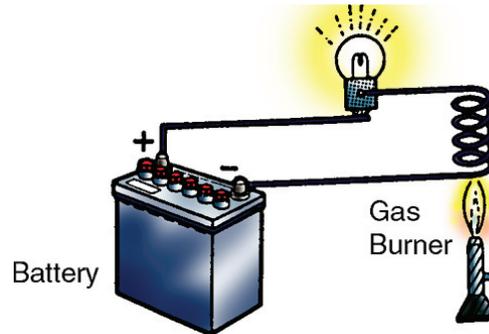
3. In most conductors, resistance increases as wire temperature increases because electrons move faster and create heat. In most insulators, resistance decreases as temperature increases. Various test equipment can be used to measure temperature and resistance.



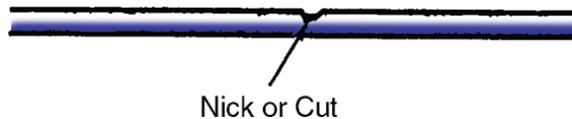4. Partially nicked or cut wire has high resistance in the damaged area. A kink in the wire, poor splices, and loose or corroded connections also increase resistance.



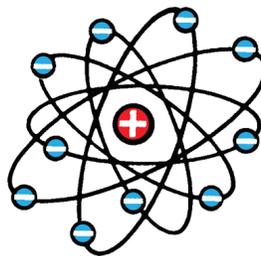5. Materials with free electrons are good conductors and have low resistance to current flow. Materials with bound electrons are insulators (poor conductors) and have high resistance to current flow.




NOTE: Copper, aluminum, gold, and silver are good conductors. Rubber, glass, paper, ceramics, plastics, and air are insulators.


ELECTRICAL/ELECTRONIC SYSTEMS

II. Stranded wire

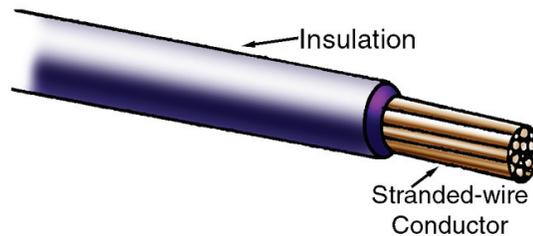- A. The stranded-wire conductor uses wire made from copper covered with polyvinyl chloride (PVC) insulation. The PVC insulation prevents electrical shorts because the bare electrical wire does not touch other conductive materials.



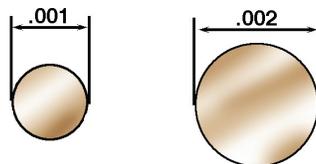1. Circuit wires must have enough surface area to carry the amount of current needed to operate the load properly. Also, they must withstand vibration and bending.
2. Stranded wire is rated according to the highest electrical current the wire can take without becoming too hot.
3. Length helps determine wire size. The greater the distance from the source of electrical current, the greater the resistance to current flow. Larger sizes of wire can counter this resistance by providing a greater number of current paths to the load.
4. The American Wire Gauge System (AWGS) and the Metric Wire Gauge System (MWGS) are used to size wire. Both of these systems assign an identification number to electrical wire based upon wire diameter.
 - a. In the AWGS, the larger the number, the smaller the wire size. Identification numbers range from 22 gauge (small) to 000 gauge (large). The cross-section of a wire is measured in a unit called a circular mil, which is the equivalent area of a circle whose diameter is 0.001 in.




- b. In the MWGS, the larger the number, the larger the wire size. Identification numbers range from 0.5 millimeters (small) to 4.0 millimeters (large).

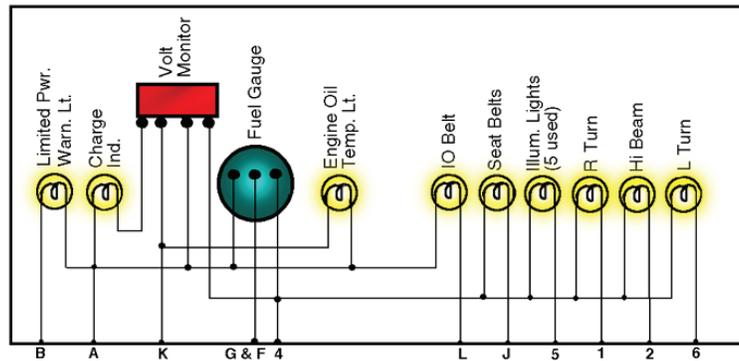5. Individual wires are bound into wiring harnesses and routed throughout the vehicle. For an orderly wiring system, manufacturers cover wires with different insulation colors.
- B. The printed circuit board is a conductor. Copper is laminated to an insulating material. The copper is processed so that it forms individual strips, each of which becomes a current path for circuits.

Printed Circuit Board



Reprinted with permission from Chrysler Motors




Schematic Symbol for Printed Circuit Board




NOTE: The copper strips in printed circuit boards are thin and should be handled with care. Check for breaks in the printed circuit board where there is a bend.

ELECTRICAL/ELECTRONIC SYSTEMS

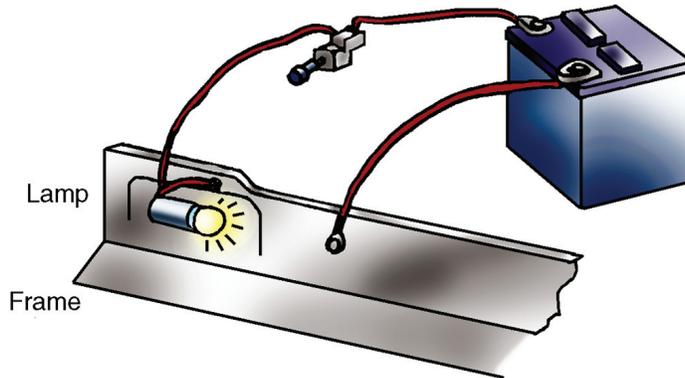
- C. If the body of the vehicle is constructed of metal, it can be a conductor. To cut costs and reduce vehicle weight, manufacturers use the steel frame and metal body as a current path for some circuits. This is referred to as chassis ground or a 1-wire system.



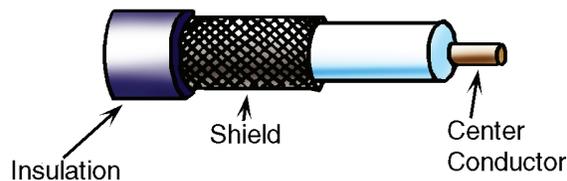- D. In early model cars, spark plugs were made of stranded copper wrapped in thick insulation. When radios were introduced, a change in spark plug wire construction became necessary.
1. The force of electron flow is so great in spark plug wires that it causes a popping noise in the radio. To eliminate this noise, manufacturers use radio suppression wires in spark plugs.
 - a. Radio suppression wires are fiberglass cords saturated with carbon. Heavy silicone or vinyl insulates the central cord.
 - b. Because carbon is not as good of a conductor as copper, radio suppression wires generate less radio interference.
 2. Special care should be taken when removing and installing spark plug wires. If stretched, the fiberglass cord within the spark plug wire can be easily damaged.



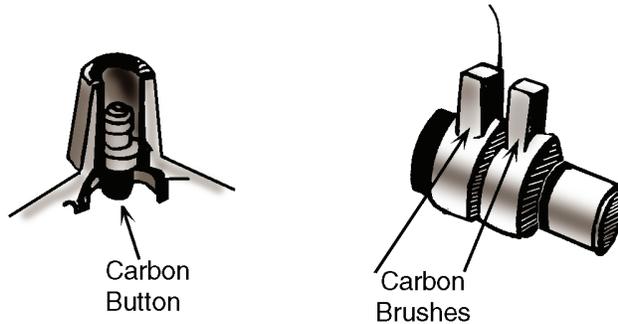- E. Carbon is used in a variety of conductors. It has a higher resistance to current flow than other conductors. Also, carbon can maintain current flow between stationary and rotating parts and resist wear that results from rubbing.




III. Types of electrical insulation

- A. Electrical insulation keeps electron flow inside the conductor and prevents different conductors from making contact. PVC is the most common type of electrical insulation.


NOTE: Insulation devices can be deceptive. A flat washer can be an insulation device. The technician must know where current is supposed to flow within a circuit.

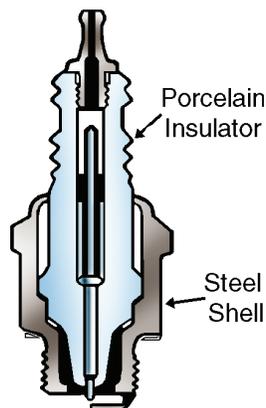- B. Glass and porcelain are used as insulation devices because they maintain resistance at high temperatures. These materials are used in spark plugs, oxygen sensors, and other applications that involve high temperatures and high voltage.




ELECTRICAL/ELECTRONIC SYSTEMS

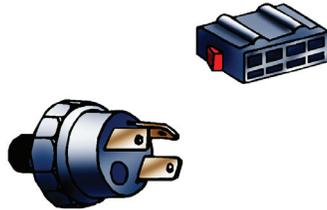- C. Bakelite, plastic, and alkyd are used as rigid insulation devices because they can be molded into almost any shape. A conductor can be embedded into these materials or placed in them after molding. The following are examples of how rigid insulation devices are used in different areas of the vehicle.



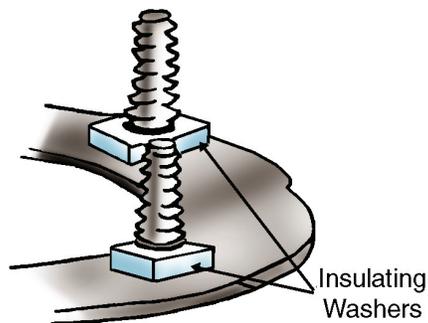
- D. Insulating washers prevent current from grounding as it passes through other conductive materials. The following shows a stud inserted through the aluminum housing of an alternator. The insulating washers keep the stud from contacting the aluminum housing.




- E. Conductors that lie close to each other are often coated with varnish to ensure that current does not leak from one conductor to the other. Any wrapped coil is coated with varnish.

IV. Types of circuit protection devices

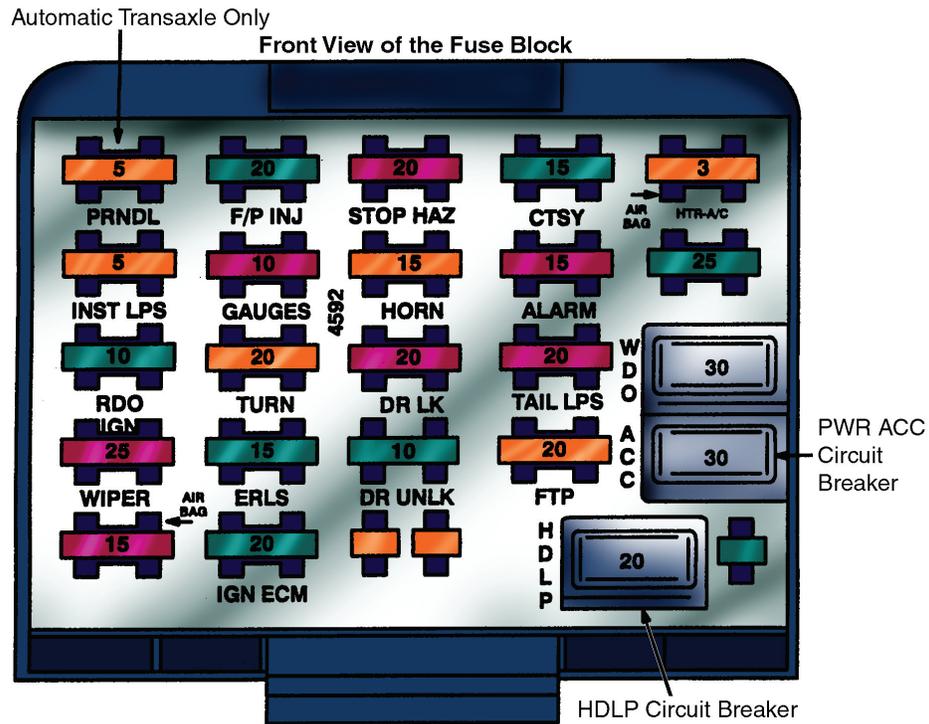- A. Fuses, fusible links, and circuit breakers are located in the fuse block. These devices are designed to open the circuit when excess current flows through.



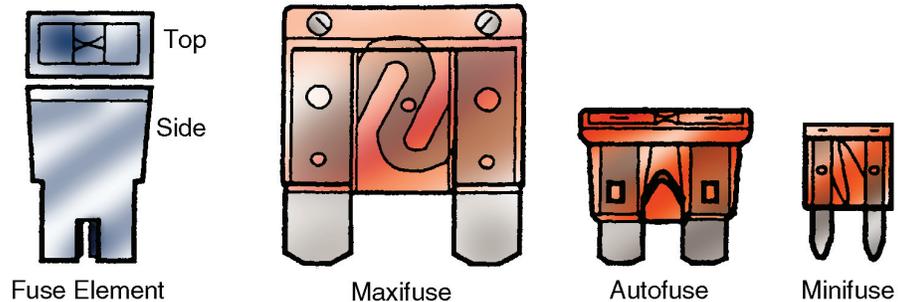
- B. The fuse is a zinc strip bonded between two endcaps. The zinc strip is encased in glass, plastic, or a ceramic sleeve. It is designed to destruct at a specific ampere of current flow.



1. Fuses are categorized by a letter system and number. The number indicates the maximum current-carrying capacity.

ELECTRICAL/ELECTRONIC SYSTEMS

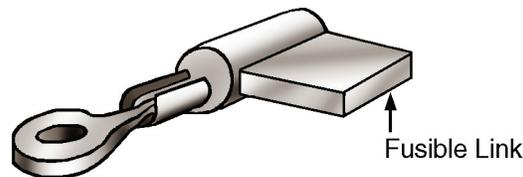2. The appearance of a blown fuse can indicate the cause of a circuit overload.
 - a. Small breaks in the zinc strip indicate a high-voltage surge or momentary current overload.
 - b. Large breaks in the zinc strip indicate a high-current overload, grounded conductor, or shorted load.
 - c. Vaporized breaks in the zinc strip indicate a grounded circuit.
- C. The fusible link is a short piece of alloyed wire. The alloy causes the fusible link to destruct at a specific ampere of current flow.




1. Fusible links are rated by wire gauge size and amperes.
2. Fusible links are usually located near the terminal connection to the power source. Fusible links sometimes have a molded flag at the terminal end, indicating gauge size and ampere rating.
3. Locating a blown fusible link can be difficult. Insulation surrounding a destroyed fusible link appears undamaged even though the insulation can be somewhat soft. The break can be located by squeezing or pulling gently on the wire.

CAUTION: Do not bypass a blown fusible link to restore a circuit. Replace the fusible link with wire that is the correct gauge and appropriate length.

- D. The circuit breaker is a thermally operated device.
 1. A bimetal strip keeps contact points on the circuit breaker closed.
 - a. When current flow through the bimetal strip becomes too great, it overheats and bends to open the contact point and disrupt circuit operation.



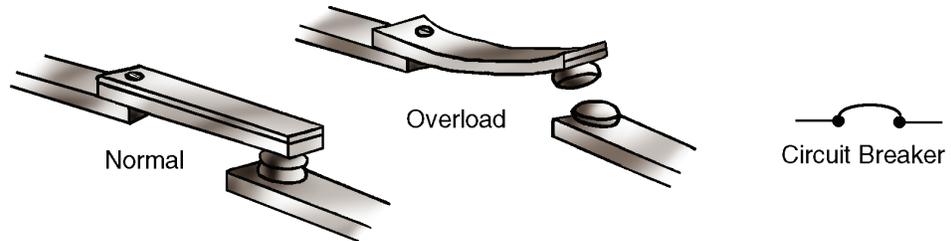- b. When the bimetal strip cools, it contracts and closes the contacts to reactivate the circuit.
- c. If circuit overload persists, the circuit breaker again overheats and opens, causing the circuit to be intermittently on and off. Continuous action of the circuit breaker can result in premature failure.




- 2. Circuit breakers are rated according to their maximum current draw before opening.
- 3. Manual circuit breakers can be reset in two ways. One way is to push a button located on the circuit breaker. The other way is to disconnect power to the circuit breaker and wait for it to cool down.

A

Side View
(external)


Side View
(internal)

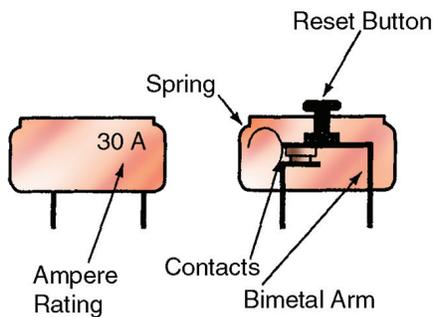


B

Side View
(external)

Side View
(internal)

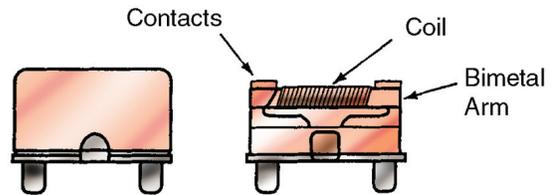

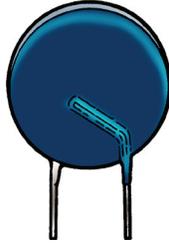
4. The positive temperature coefficient (PTC) circuit breaker is wired inside a load component like a wiper motor or power window motor. When current exceeds design limits, resistance of the PTC circuit breaker increases until the circuit is opened. The PTC circuit breaker resets once the high current condition of the circuit is no longer present.



V. Circuit load devices and how they function


- A. An electrical component must meet three requirements to be considered a load device.
 1. The device must have some current resistance to ensure the force device is not depleted too rapidly.
 2. The resistance of a load device must not be great enough to prevent current flow within the circuit.
 3. The load must perform some observable function, such as producing light, heat, or magnetism.
- B. Incandescent bulbs are the most common source of light in a vehicle. Incandescent bulbs are illumination loads.
 1. Incandescent bulbs are either single filament or multiple filament.
 - a. A single-filament incandescent bulb has one insulated contact. The bulb is grounded through its socket. In a smaller single-filament bulb, a separate contact provides ground.
 - b. A multiple-filament incandescent bulb has two heating filaments. It is grounded by a socket or by a separate terminal or contact.
 2. A numbering system categorizes incandescent bulbs according to their use.

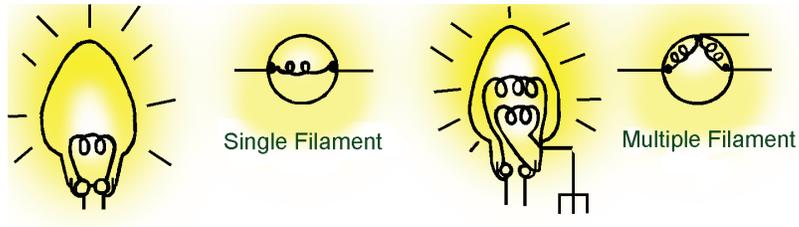3. The lower the resistance of a filament, the greater the current flow through it and the brighter the light produced.



- C. Wound coils are known as coil-wrapped loads. These are used in electrical load devices, such as starters, relays, ignition coils, wiper motors, gauges, and alternators. Wound coils function according to three basic magnetic principles.

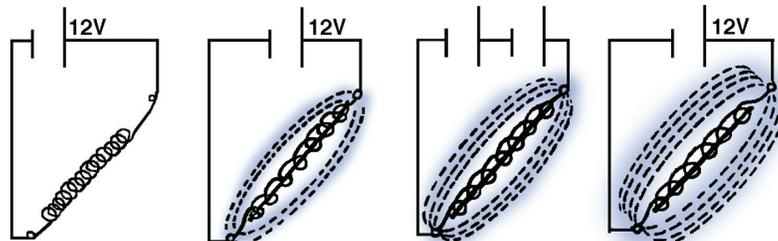1. If a current is being forced through a conductor, a magnetic field is created around that conductor.
2. To increase the strength of the magnetic field, the conductor is wrapped into a coil. Also, increasing current flow through the conductor or placing an iron core within the coil increases the strength of the magnetic field.



3. A wrapped conductor that produces a magnetic field when current passes through it is a load device.
- D. The maximum current-carrying capacity of some conductors is balanced with the amount of heat that the conductor can safely handle. The conductor produces heat as current flows. These conductors are known as thermal loads.
1. Nichrome is the most common type of thermal load. It can produce intense heat from large amounts of current flow without sustaining damage.
 2. The heat produced by thermal loads can perform a variety of functions, such as defrosting windows and operating warning gauges.

ELECTRICAL/ELECTRONIC SYSTEMS


VI. Capacitors and how they function

- A. A capacitor uses an electrostatic field to absorb or store an electrical charge.
 - 1. A capacitor in a circuit builds up a charge on its negative plate. Current flows until the capacitor charge and power source are equal. The capacitor charge is then stored until it is discharged through another circuit.

CAUTION: Handle capacitors with care. Once charged, they can cause shocks long after power is removed.


- B. The three types of capacitors are the ceramic, paper and foil, and electrolytic.
 - 1. The ceramic capacitor is used for electronic circuits.

Ceramic Capacitor

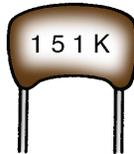


- 2. The paper and foil capacitor is used for noise containment in charging and ignition systems.

Paper and Foil Capacitor

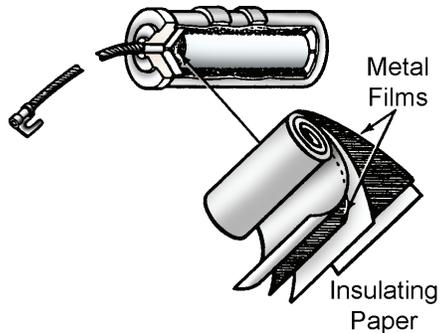

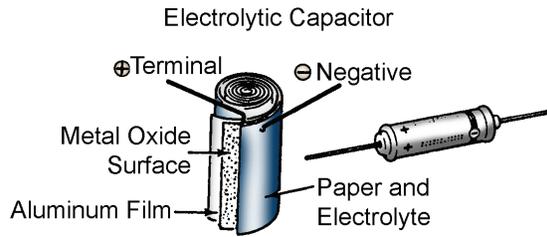3. The electrolytic capacitor is used for turn signal lights.




- C. Capacitors are rated in microfarads. The rating is stamped on the case. Make sure to choose the proper capacitor rated for the maximum expected voltage.

Capacitance	Basic Unit	Units for Small Values	
Symbol	F	μF	pF
Pronounced as	Farad	Microfarad	Picofarad
Multiplier	1	1×10^{-6} (1/1,000,000)	1×10^{-12} (1/1,000,000,000,000)

- D. A resistor is a mechanical or semiconductor device that reduces the electrical force in a circuit. All loads reduce electrical force to some degree.

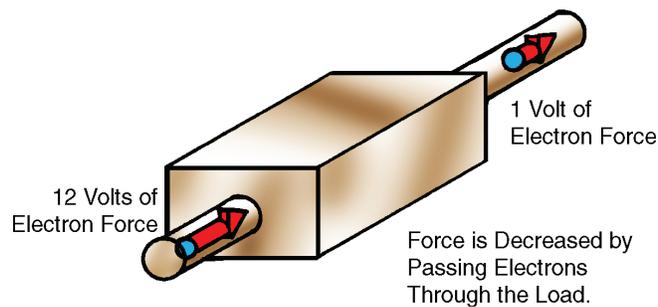1. The force reduction across a load is called voltage drop. When electrons are forced through a coil, light bulb, or heater, they are converted into magnetism, heat, light, or motion.




2. The resistor causes voltage drop to occur across itself. It differs from other load devices because its single purpose is to produce voltage drop, causing the circuit to operate at lower voltage.




NOTE: Heat and magnetism produced by the resistor have no practical use.

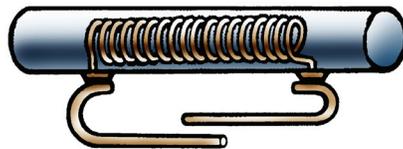3. The three classifications of resistors are fixed-value, stepped, and variable.
 - a. The two types of fixed-value resistors are wire-wound and carbon.
 1. Wire-wound resistors are made with coils of resistance wire. They are accurate and heat stable. The resistance value is marked on them.



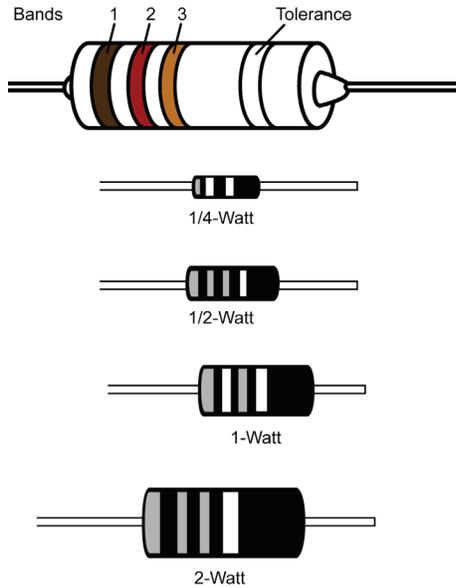2. Carbon resistors are mixed with binder. The more carbon, the lower the resistance. Some have the resistance value stamped on them while others are rated in watts of power. Most have color-coded bands to show resistance value. A carbon resistor with four bands – red, green, black, and brown from left to right – is sized as follows:
 - The first two bands set the digits. Red is 2 and green is 5.
 - The next band represents the number of zeros. Black is 0 zeros. So, the resistor has a base value of 25W.


- The last band represents tolerance. Brown is 1%. So, the resistance value is 25 ohms plus or minus .25 ohms, or 24.75W to 25.25W.



Band 1 1st Digit		Band 2 2ndDigit		Band 3 (no. of zeros)	
Color	Digit	Color	Digit	Color	Digit
Black	0	Black	0	Black	0
Brown	1	Brown	1	Brown	1
Red	2	Red	2	Red	2
Orange	3	Orange	3	Orange	3
Yellow	4	Yellow	4	Yellow	4
Green	5	Green	5	Green	5
Blue	6	Blue	6	Blue	6
Violet	7	Violet	7	Violet	7
Gray	8	Gray	8	Gray	8
White	9	White	9	White	9


Resistance Tolerance	
Color	Tolerance
None	±20%
Silver	±10%
Gold	± 5%
Red	± 2%
Brown	± 1%

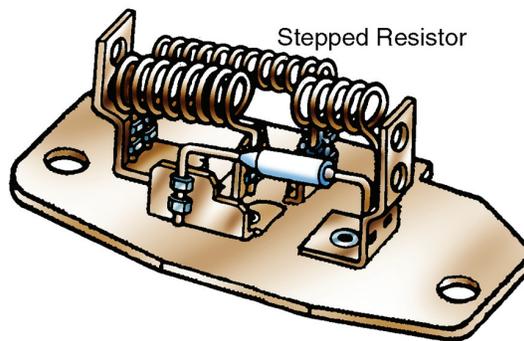- b. Two or more fixed resistance values are contained in stepped or tapped resistors. The different resistances, which are either carbon or wire, are connected to different terminals in a switch. Different resistance values are placed in the circuit as the switch is moved.




- c. The three types of variable resistors are rheostats, potentiometers, and thermistors.

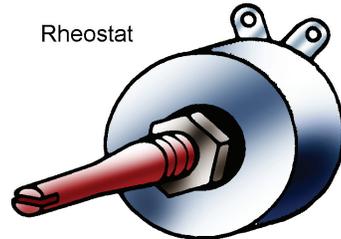1. The rheostat dims or brightens the dash panel lighting and is located on the headlight switch. One end of the rheostat is connected to the fixed end of a resistor. The other end is connected to a sliding contact on the resistor. Rotating the control increases or decreases resistance.



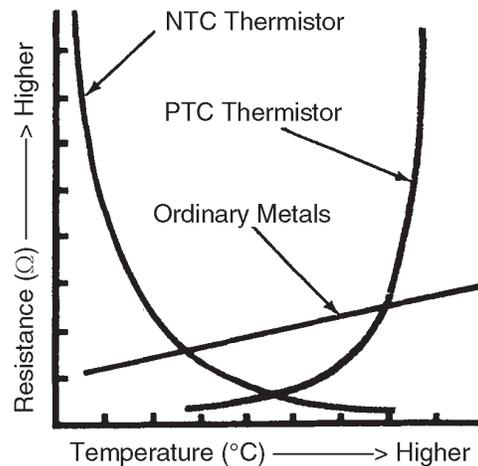2. The potentiometer is a device that varies resistance according to the movement of mechanical parts. The first two connections of a potentiometer are made at each of the resistor ends. The last connection is made on a sliding contact. Rotating the control increases or decreases resistance in the circuit.
3. The thermistor is a device that varies resistance according to temperature. Negative temperature coefficient (NTC) thermistors and positive temperature coefficient (PTC) thermistors can be used in the same vehicle.
 - Each of these thermistors change resistance with an increase in temperature. In NTC thermistors, resistance decreases as temperature increases. In PTC thermistors, resistance increases as temperature decreases.




VII. Circuit control devices and how they function

- A. A circuit control device controls the amount of current flowing through a circuit. It also ensures that current flows at the proper time. A circuit control device performs one of three essential functions.
 - 1. The circuit control device opens or closes the circuit by mechanical or electronic means.
 - 2. The circuit control device relays a large rate of current by means of a small current signal.
 - 3. The circuit control device increases or decreases current rate.
- B. The most common circuit control device is a switch.
 - 1. The switch has two or more sets of contacts. Opening the contacts is referred to as breaking the circuit. Closing the contacts is called making the circuit.
 - 2. Poles refer to the number of input circuit terminals and throws refer to the number of output circuits.
 - a. A single-input (pole), single-output (throw) switch is called a single-pole, single-throw switch (SPST).
 - b. A single-input (pole), double-output (throw) switch is called a single-pole, double-throw (SPDT) switch.
 - c. A multiple-input (pole), multiple-output (throw) switch is called a multiple-pole, multiple-throw (MPMT) switch.
 - 3. Switches can be push-pull, rotary, or momentary on/off.


ELECTRICAL/ELECTRONIC SYSTEMS

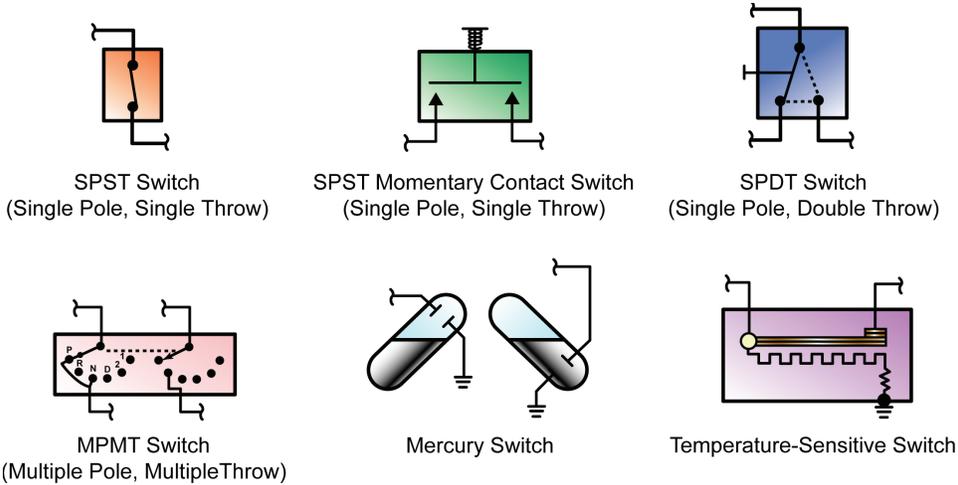4. The six different types of switches are the SPST, SPST momentary contact, SPDT, MPMT, mercury, and temperature-sensitive.




- C. A relay is a remote-control switch that uses a small amount of current to control a large amount of current. A standard relay has a control circuit and a power circuit.


Construction

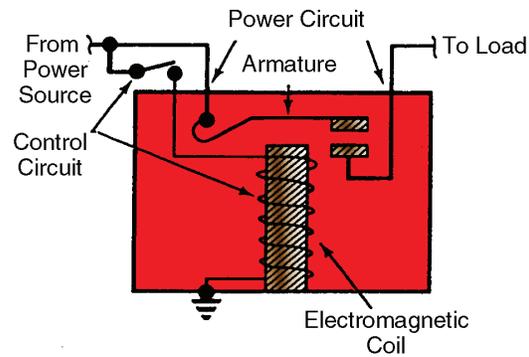


Operation

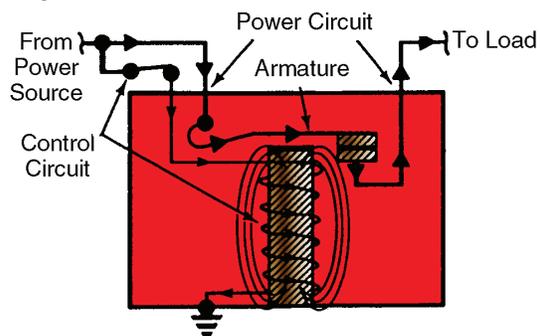

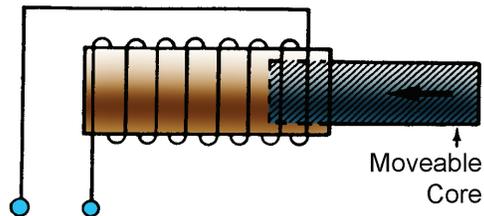
1. The power source supplies current to the control circuit. Current then flows through a switch and an electromagnetic coil to ground.
 2. The power source supplies current to the power circuit. Current flows to an armature, which can be attracted by the magnetic force on the electromagnetic coil.
- D. A solenoid is an electromagnetic switch that has a moveable core to convert current flow into mechanical movement.



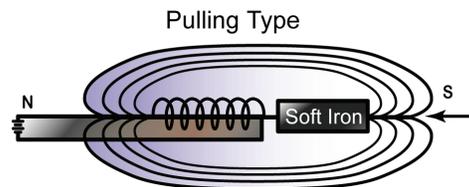1. In the pulling-type solenoid, the magnetic field pulls the core into a coil. A pull-in coil pulls the core into the coil, and a hold-in coil holds the core in place.



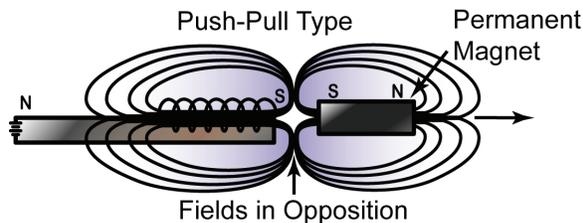
2. In a push-pull-type solenoid, a permanent magnet is used for the core. By changing current flow direction, the core is pulled in or pushed out. This type of solenoid is used on electric door locks.



- E. Comfort and convenience luxuries are provided using electronic devices and systems called solid-state electronics. These work through the control of electricity and do not have electromechanical parts.


ELECTRICAL/ELECTRONIC SYSTEMS

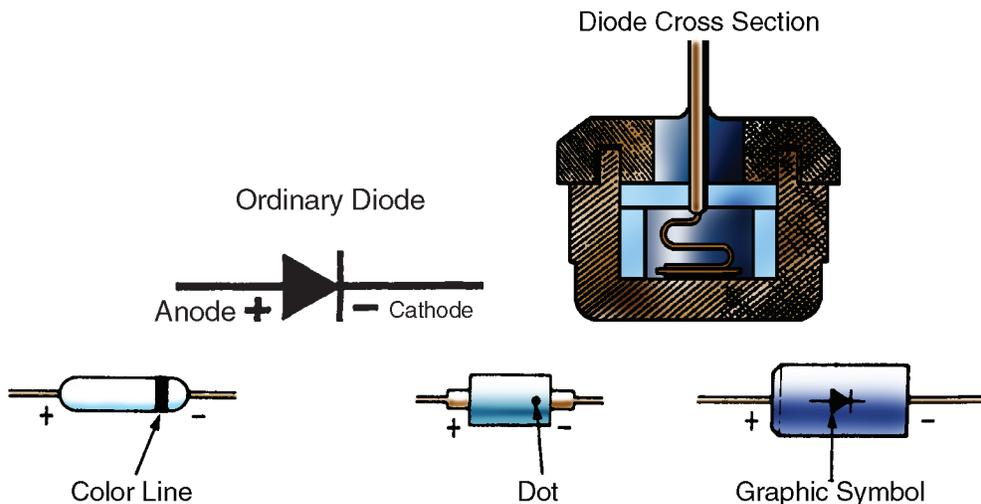1. Current flows through a semiconductor. This movement produces an electrical signal that may be transmitted, amplified, or utilized in special circuits in order to perform logical decision-making functions.
- F. Semiconductors have the ability to act like conductors or insulators. While their resistance is higher than conductors like copper or iron, it is lower than insulators like glass or rubber. Semiconductors have special electrical properties.
1. By mixing certain substances, conductivity can be increased.
 2. Light, temperature, and mechanical pressure can alter resistance.
 3. By passing current through semiconductors, light is produced.
- G. The diode controls the direction of current flow but not the rate of current flow. The diode acts as a one-way electron check valve that allows current flow in one direction but stops current flow coming from the other direction.



- H. The zener diode is similar to the diode.
1. Under normal conditions, the zener diode allows current flow in one direction and stops current flow in the opposite direction up to a point.
 2. If opposing current flow is forced hard enough, the zener diode will break down, allowing current flow in either direction.
 3. When the opposing current flow decreases, the zener diode again functions as a diode.

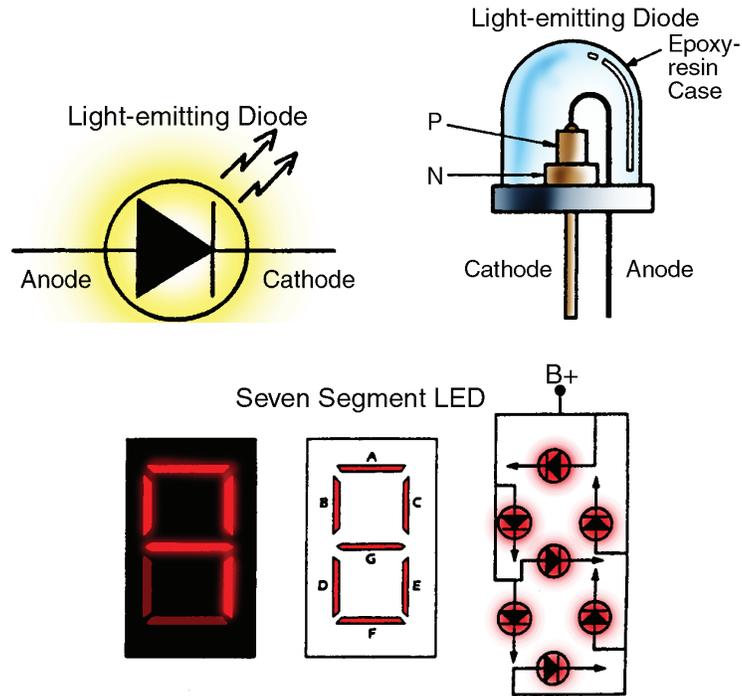- I. The light-emitting diode (LED) is a diode that produces light. Transparent epoxy cases are produced with LEDs, so they can emit the light they generate when forward biased. Depending on how the material is doped, the color of the light given off by a LED can be red, green, or infrared.




1. As in a diode, the LED allows current flow in only one direction.
 - a. The forward bias voltage drop is 1.5 volts to 2 volts, which is much higher than a diode.
 - b. The forward bias current through the LED must be kept under control or damage will result.
2. Some advantages of LEDs are longer life, cooler operation, lower voltage requirements, and the ability to produce the same amount of light as an incandescent bulb while using less power.

VIII. Transistors and how they function

- A. Transistors are made from positive-type (P-type) and negative-type (N-type) materials. They utilize the same principles as the diode. Transistors have two positive/negative junctions.


ELECTRICAL/ELECTRONIC SYSTEMS

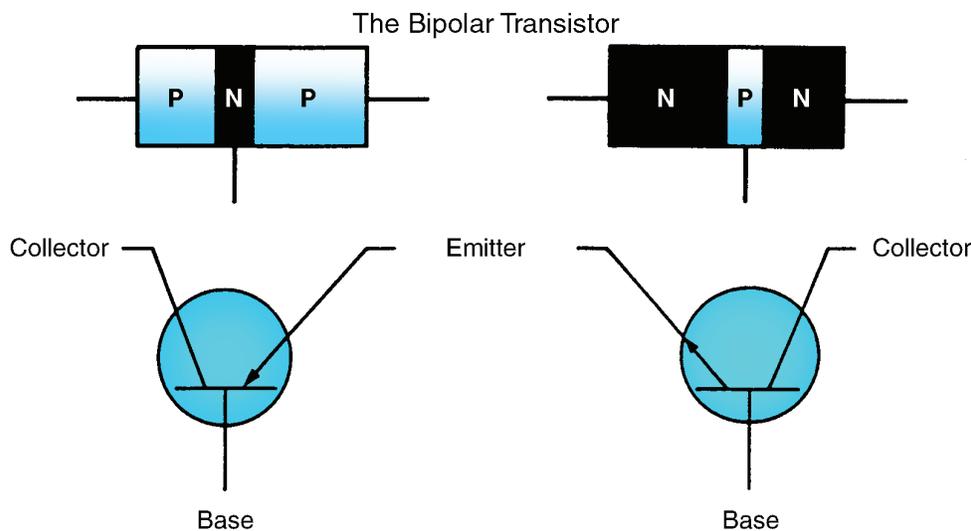1. A transistor performs more functions than a diode, such as operating as a solid-state switch or amplifier. When used in a vehicle, the transistor is most commonly used as a switch.
 - a. Transistors, such as the AC blower motor, are used as amplifiers to control the speed of the electric motor.
 - b. Transistors are used as solid-state switches to control actuators, such as electronic fuel injectors.
- B. The three parts of a bipolar transistor are the emitter, base, and collector.
 1. The two types of bipolar transistors are the positive-negative-positive (PNP) and the negative-positive-negative (NPN). Transistor type is determined by the type of material used to make each of the three transistor parts.



- a. In the PNP transistor, the emitter is made from P-type material, the base is N-type material, and the collector is P-type material. In order for the PNP transistor to operate, the emitter must be connected to negative, the base to positive, and the collector to negative.
- b. In the NPN transistor, the emitter is made from N-type material, the base is P-type material, and the collector is N-type material. In order for the NPN transistor to operate, the emitter must be connected to positive, the base to negative, and the collector to positive.

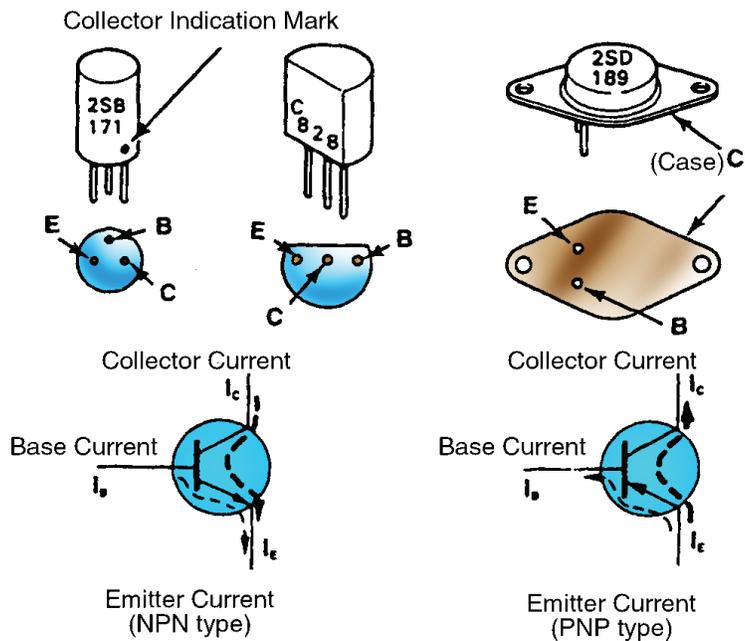2. PNP and NPN transistors function the same way. Both of the transistors possess a forward-biased junction and a reverse-biased junction.
3. Current flow between the emitter and base controls current flow between the emitter and collector.
 - a. The emitter is the most heavily doped. It has the most excess electrons or holes, depending on whether the emitter is P-type or N-type material.
 - b. The collector is doped slightly less than the emitter. The base is thin with the fewest doping atoms.
 1. As a result of doping, current flow in the emitter-collector is much greater than in the emitter-base.
 2. By regulating current at the emitter-base junction, the amount of current allowed to pass from the emitter to the collector is controlled.




ELECTRICAL/ELECTRONIC SYSTEMS

IX. Integrated circuits

- A. An integrated circuit (IC) connects transistors, diodes, capacitors, and resistors with conductors built onto one silicon chip. Due to the compact design, the IC reduces the number of contact junctions, cost of production, and consumption of power. The IC is classified by the number of parts included on one chip.

Chip Containing Integrated Circuits

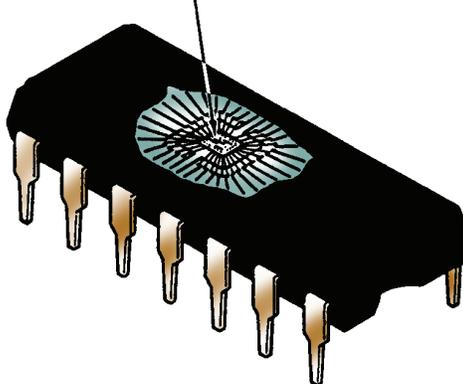

X. Logic Circuits


- A. Logic circuits consist of transistors combined in units called gates. Gates are switches powered by voltage that process signals logically based on digital on/off language.

NOTE: Logic circuits are represented by logic symbols to aid in the understanding of the circuit. These logic symbols are used to show the internal circuits of computers and solid-state control modules and are helpful when analyzing wiring damage.



- The AND gate is a circuit with two series switches. Both switches must be closed for the circuit to operate.


Logic Symbol for AND Gate

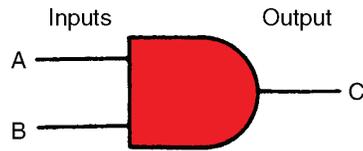


Truth Table for AND Gate

Inputs		Output
A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Actual Semiconductor AND Circuit

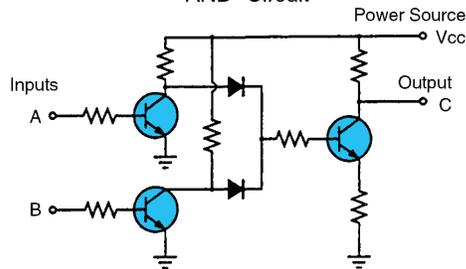


Equivalent Mechanical Circuit

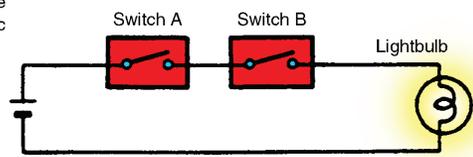

- The OR gate is a mechanical circuit with two parallel switches. If either switch is closed or both are closed, the circuit will operate.


Logic Symbol for OR Gate

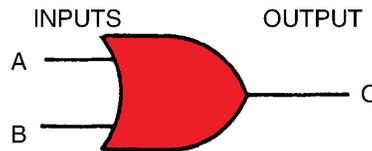


Truth Table for OR Gate

Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

Actual Semiconductor OR Circuit

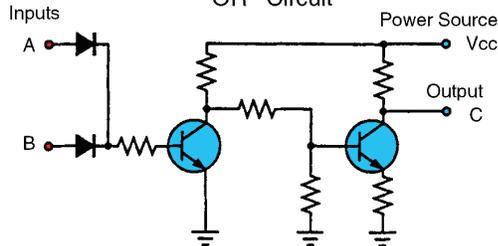


Equivalent Mechanical Circuit

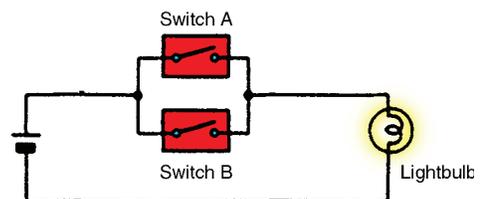

3. The NOT gate inverts voltage so that output is opposite of input.


Logic Symbol for NOT Gate

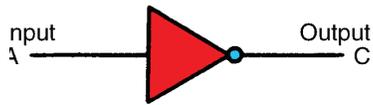


Truth Table for NOT Gate

Input A	Output C
1	0
0	1

Actual Semiconductor NOT Circuit

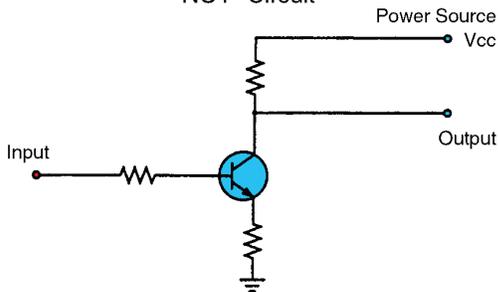


Equivalent Mechanical Circuit

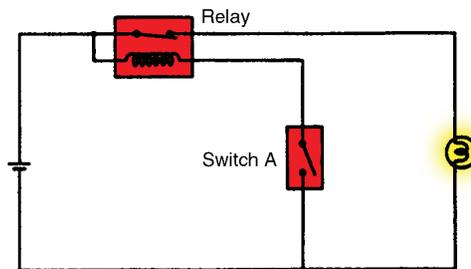


4. The NAND gate functions like an AND gate with an opposite output. The output is on for all input conditions unless there is voltage at both inputs.

Logic Gate for NAND Gate

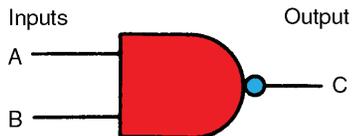


Truth Table for NAND Gate

Inputs		Output C
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

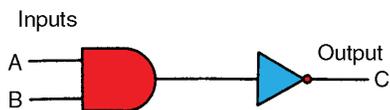


5. The NOR gate functions like an OR gate with an opposite output. The output is on if there is no voltage at both inputs.

Logic Gate for NOR Gate

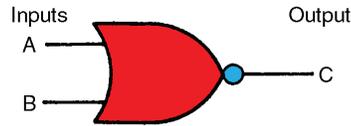


Truth Table for NOR Gate

Inputs		Output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

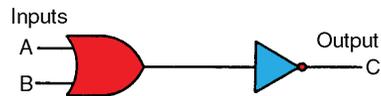

6. The XOR gate is the exclusive OR gate that limits output and is represented with an added curved line. The exclusive feature requires that an even number of ones produces a 0 (low output) while an odd number of ones produces a 1 (high output).

Logic Symbol for XOR Gate

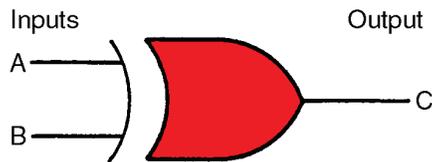

Truth Table for XOR Gate

Inputs		Output
A	B	C
0	0	0
0	1	1
1	0	1
1	1	0